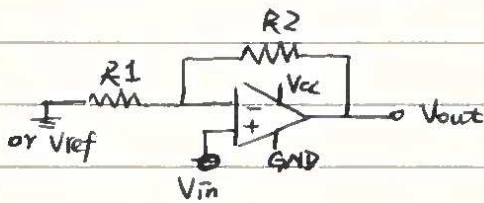


2022/07/05

Try amplifier MCP 6001 & LM741

Operational Amplifier




Typical Application


$$\text{Gain} = 1 + \frac{R_2}{R_1} = \frac{R_1 + R_2}{R_1}$$

Non-inverting

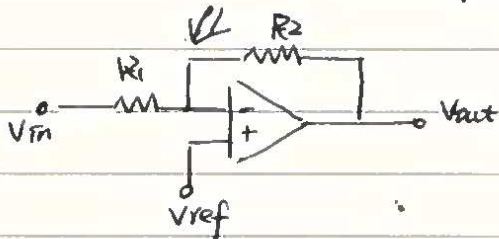when $V_+ > V_-$ increase output
when $V_- > V_+$ decrease output.



$$\text{Gain} = 1 + \frac{R_2}{R_1}$$

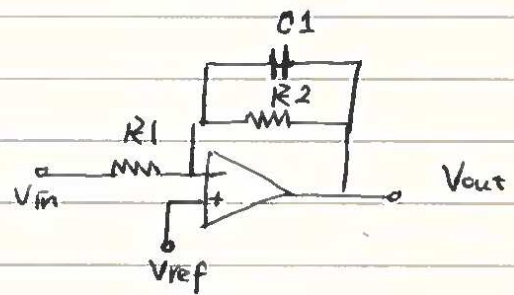


My application

(non-inverting)

(Inverting)

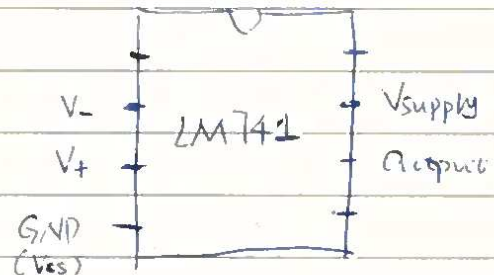
when $V_- > V_+$ thus reduce output.
when $V_- < V_+$ thus increase output



Important Discover: The input power supply \rightarrow AC instead of DC

which is discovered when using it as power supply for amplifiers.

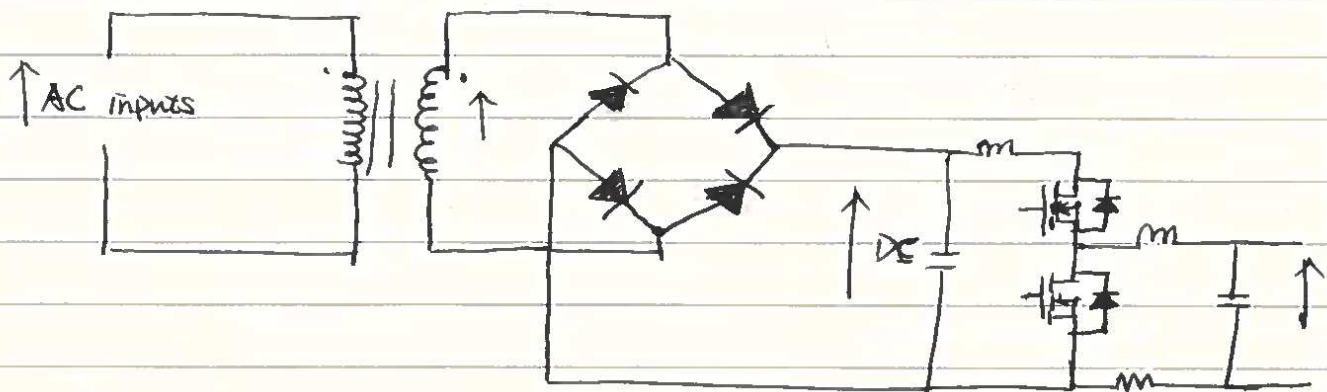Buck Converter does not have rectifier implanted between inputs and switches. (with isolation better)



rectifier with isolation

outputs has isolation design too
but this is the original design of buck converter

find LM741 Teaxes Instrument ~~LT~~ LTspice model

How to ~~pick the~~ choose an operational amplifier

Power input/output & Frequency.

V_{DD} & V_{SS} → Maximum Rating Entry (Absolute)
positive negative (GND) output within power supply.

Freq: Slew Rate / Unity Gain Bandwidth / Gain Bandwidth Product

how fast the output can change

Volts/~~ms~~ μ s (gain could affect it)

Maximum freq obtained at given gain \Rightarrow GBW

Gain \times freq (max)

if $f = 1 \text{ kHz}$ Gain = 1000

~~\Rightarrow $1 \text{ kHz} \times 1000 = 1 \text{ MHz}$ GBW~~

$\Rightarrow 1 \text{ kHz} \times \frac{1}{1000} = 1 \text{ MHz GBW}$

Here \rightarrow inputs difference 0.1mV or even smaller

output 5V $\Rightarrow \frac{5}{0.1 \text{ mV}} = 10000 \times 5 = 5 \times 10^4$ Gain

$5 \times 10^4 \times 2.25 \text{ M} \rightarrow 11.25 \times 10^4 \text{ MHz}$
112.5 GHz GBW

LT1413 \rightarrow work well in LTspice

\checkmark V_{DD} = 5V \rightarrow input 10mV \rightarrow output Id = 1A
(10m Ω R_{sense})
0.3V/ μ s

LM741 \rightarrow X \rightarrow cannot support 4.7V output by the same circuit

\checkmark \rightarrow only give 3.6V output \rightarrow 30mA Id.
0.5 or 0.7V/ μ s