

FDSPP26A — 0.12V — 33A)^{(on}

0.1A at 1V source voltage.

1.2V ~ 1.5V Gate voltage


for LM741 & FDSPP26A.

$$\begin{aligned} \approx 1 \quad V_{ref} &= \frac{1 + [1.2 \sim 1.5]}{2} \\ &= \frac{2.2 \sim 2.5}{2} \\ &= 1.1 \sim 1.25 \text{ V} \end{aligned}$$


by simulation, the feed V_{in} from R_{sense} .

V_{ref} should be 0.6 ~ 1.8 V to get 0.1A ^{I_{d1}} output

Constant Resistance

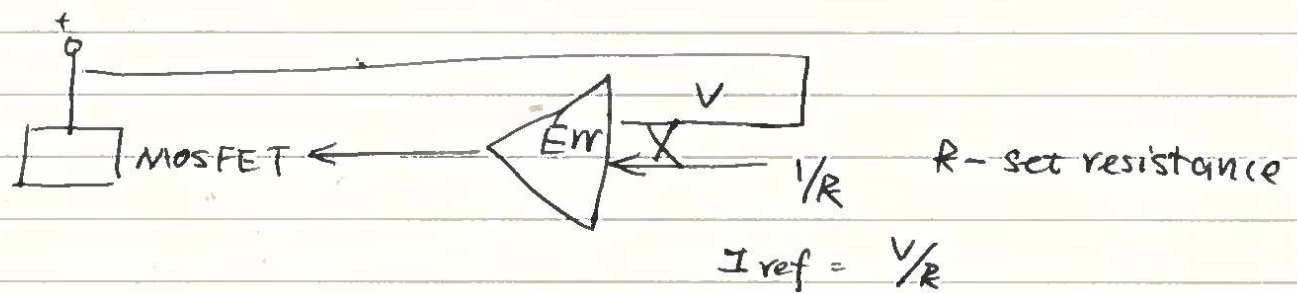

Constant Resistance Mode

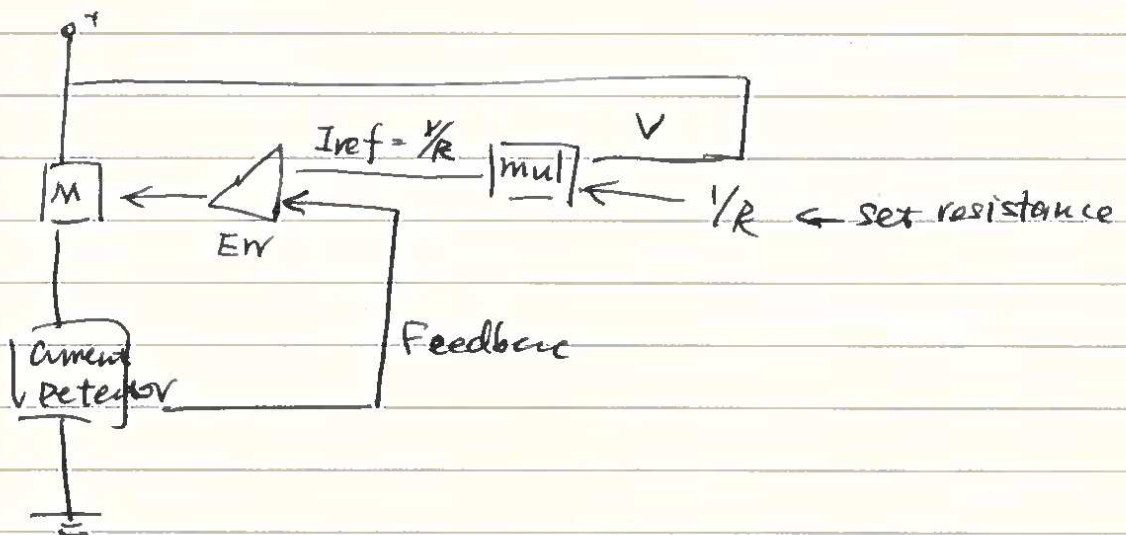

for example, we want this electronic load act as a constant resistor with 2Ω resistance.

$$\begin{array}{l} \rightarrow 1V \text{ source } \quad \frac{1}{2} = \frac{1}{2}A = 0.5A \\ \rightarrow 2V \text{ source } \quad \frac{2}{2} = 1A \end{array} \quad \left. \vphantom{\begin{array}{l} \rightarrow 1V \text{ source } \\ \rightarrow 2V \text{ source } \end{array}} \right\} \begin{array}{l} \text{sense} \\ \text{resistor} \end{array} \rightarrow \begin{array}{l} 0.5V \\ 1V \end{array}$$

Multiplexer $\rightarrow \frac{1}{2} \rightarrow R$

$V_{\text{control}} \rightarrow \frac{0.6 \sim 1.8V}{0.2 \sim 2.6V} \rightarrow 1.2V$

Comparator.

~~AA~~ $-0.5+$


Amplifier \rightarrow only amplifying the AC part of signal & DC part of sig which amplification on DC part have trouble to have require additional control to balance

$\rightarrow V_- \rightarrow V_{\text{in}}$ from current sense amplifier has DC part

$\rightarrow V_+ \rightarrow V_{\text{ref}}$ from set source voltage

Precision Amplifier \rightarrow reduce.

MAX44280.

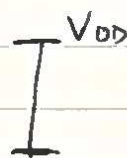

Common voltage.

~~$V_{\text{in}} + V_{\text{O}} + 0.1m$~~

Comparator

0,01V

$$V_{in} = 7V + 1mV \sin t \quad 0,989V \quad 0,969V \quad 20mV \rightarrow 10mV \sin t + 0,999V$$

