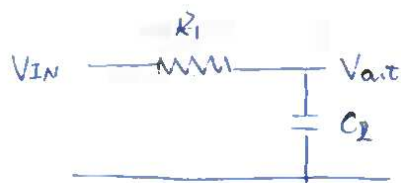


RC Filter → How much voltage can be passed?

Is there any attenuation?



PWM signal with 7.32 Hz

$$V_{OUT} = V_{IN} \left(\frac{R_2}{R_1 + R_2} \right)$$

$$= V_{IN} \times \left(\frac{X_C}{\sqrt{R_1^2 + X_C^2}} \right)$$

$$X_C = \frac{1}{2\pi f C}$$

↑
freq.

$$V_{OUT} - 1Hz = V_{IN} \times \frac{\frac{1}{2\pi \times 1 \times C}}{\sqrt{R_1^2 + \frac{1}{4\pi^2 \times 1 \times C^2}}}$$

let's say 10kΩ & 10μF

10kΩ & 1μF > 1.5fHz cut-off.

$$V_{OUT} - 1Hz = V_{IN} \times \frac{\frac{1}{2\pi \times 1 \times 10^{-6}}}{\sqrt{(10^4)^2 + \frac{1}{4\pi^2 \times 1 \times 10^{-12}}}}$$

in Hz

$$= V_{IN} \times \frac{\frac{1}{2\pi \times 10^{-5}}}{\sqrt{10^8 + \frac{1}{4\pi^2 \times 10^{-10}}}} = 0.8467 V_{IN}$$

at 1Hz

at 0.1Hz 0.001Hz

$$\rightarrow \frac{\frac{1}{2\pi f \times 10^{-5}}}{\sqrt{10^8 + \frac{1}{4\pi^2 f^2 \times 10^{-10}}}} = 1 \sim \text{Amplitude} \times \text{duty}$$

$$Z = R_1 + \frac{1}{2\pi f C_2}$$

$$P = I^2 Z = \frac{V^2}{Z} = \frac{V_{in}^2}{R_1 + \frac{1}{2\pi f C_2}}$$

as small as possible

$$P_{max} = \frac{V_{in}^2 \times 2\pi f C_2}{1} \approx 0$$

$$P = \frac{V_{in}^2}{R_1 + \frac{1}{2\pi f C_2}} \xrightarrow{\text{at } f \rightarrow \infty} P = \frac{V_{in}^2}{R_1}$$

as big as possible

therefore small R

Small R → good filtering at high ~~voltage~~ freq

small C → good passing at small freq ✓

pick big R & small C → good at small freq.

↓
add more stages small current → small losses

```

#include <Wire.h>
#include <LiquidCrystal_I2C.h> //Download it here: https://www.electrooons.com/eng_arduino_liq_crystal.php
////////////////////////////////////Library for ADS1115 ADC////////////////////////////////////
#include <Adafruit_ADS1015.h> //Download here: https://www.electrooons.com/eng_arduino_adafruit_ADS1015.php
Adafruit_ADS1115 ads(0x48); //Define i2c address
////////////////////////////////////

// Sometimes the address is 0x27 or 0x3f (try both)
LiquidCrystal_I2C lcd(0x27, 16, 2); //Address, columns, rows

const float multiplier = 0.0001875; //In order to pass from 16bits to real value voltage
int Buzzer = 3; //Pin for a buzzer (not yet used)
float offset = 0.004; //Constant offset (in A) that the read has (yours might be different)

void setup() {
  Serial.begin(9600);

  pinMode(Buzzer, OUTPUT);
  digitalWrite(Buzzer, LOW);

  ads.begin();
  delay(10);

  lcd.init();
  lcd.backlight();
  lcd.clear();
  lcd.setCursor(0, 0);
  lcd.print(" ELECTROOONS ");
  analogWrite(Buzzer, 200);
  delay(100);
  analogWrite(Buzzer, LOW);
  delay(300);
  lcd.setCursor(0, 1);
  lcd.print(" CONSTANT LOAD ");
  delay(1500);
}

void loop() {
  float set_val, real_val;
  real_val = ads.readADC_Differential_0_1(); //Read DIFFERENTIAL voltage between ADC0 and ADC1
  set_val = ads.readADC_SingleEnded(2); //Read voltage on potentiometer (this will be our setpoint)

  set_val = (set_val * multiplier) - offset; //Pass to real voltage and subtract offset
  real_val = real_val * multiplier - offset;

  //If we have negative value, we stay at 0.
  if(real_val < 0)
  { real_val = 0; }
  if(set_val < 0)
  { set_val = 0; }

  //Print data on LCD
  //lcd.clear();
  lcd.setCursor(0, 0);
  lcd.print("Set: ");
  lcd.print(set_val, 3);
  lcd.print(" A");
  lcd.setCursor(0, 1);
  lcd.print("Current: ");
  lcd.print(real_val, 3);
  lcd.print(" A");
  delay(100);
}

```

Gain (10)
5 ~ 1.25V

for 4 stages
→ 4A ~ 2A
for one stage
→ < 2A

1A ~ 0.25A per branch
0.5V ~ 0.125V Use
current sense amplifier
Gain (10)

0.5V
30.3 × 0.5 = 15.15mV

for 1/2
30.3mV
→ Gain → 10 → 303mV
Gain → 20 → 606mV ✓
Gain → 60 → 1.818V ✓
Gain →

20 ~ 30 gain → 40 ~ 60.
But for high current.

4A → 1A per branch.
↓
0.5V → max input V = 10V
20 max gain