
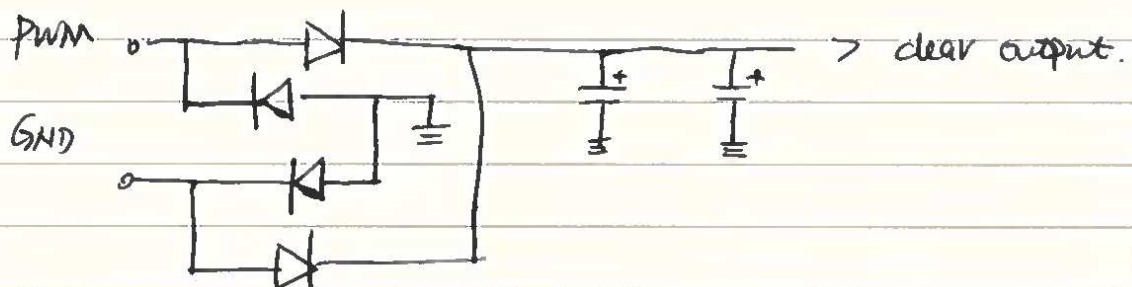


2022/07/10.

Good resolution
but add capacitors
to remove oscillations

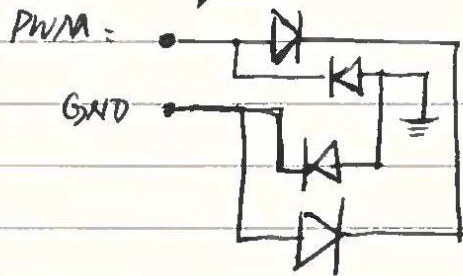Common Current \rightarrow V_{ref} can be controlled by Arduino
or V_{ref} controlled by potentiometer \leftarrow Arduino
(resolution - problem)



Power resistor 0.22 Ω 5W 0.68 Ω 5W 1 Ω 5W

Common Resistance \rightarrow V_{ref} controlled by V_{source}

$$V_{ref} = \text{ratio} \times V_{source}$$

$$= \frac{R_{power}}{R_{set}} \times V_{source}$$

if $R_{power} = 1 \Omega \rightarrow$ cannot reach $\frac{1}{4}$ Ω resistance.



$$V_{ref} = V_{source}$$

if $R_{power} = 0.68 \Omega \rightarrow \frac{0.68}{1} \times V_s = \frac{68}{100}$

0.25 minimum resistance.

0.1 0.22 0.33 0.68 1.2
0.47