

Circuit Design

① MOSFET — Electronic Load

V_{out+} & V_{out-}

LM324 → V_{ref} vs V_{sense} (0V ~ 12V power supply)

LM324, PWM filter + voltage follower

4 stages & 1 stages

AD623AN → Instrumentation Amp (0 ~ 12V power supply)

$$V_{power resistor} \times 5 \text{ (gain)} = 2.5V \rightarrow V_{sense}$$

(0 ~ 0.5V for 0.5A)

↓
1A max

$$V_{power resistor} \times 6 \text{ (gain)} = 3V$$

② Sense ADS1115 system.

→ V_{out+}
→ V_{out-}
→ V_{sense} (be amplified)
→ V_{ref} (be filtered)

} ADS1115
0x48

→ V_{temp1}

→ V_{temp2}

→ V_{temp3}

→ V_{temp4}

} ADS1115
0x49

$$Temp_avg = \frac{V_{temp1} + V_{temp2} + V_{temp3} + V_{temp4}}{4}$$

⇒ 4 stages ✱

$$Temp_avg = V_{temp1}$$

⇒ 1 stage.

(1 stage thermal analysis
✱ not a big problem)

③ Arduino Control

- ① ADS1115 measurement SDA & SCL
- ② LCD Display SDA & SCL
- ③ 1 or 4 stage Control → Rely
- ④ short circuit Control → Rely
- ⑤ PWM output → V_{ref}
- ⑥ Fan Control → turn on MOSFET

} I²C communication
(Addresses)

PCB Modification.

↓
Separate - stack PCB (Heat concern)

Track ~~cross~~ cross - separate 1, 4 stages Electronic Load

separate Electronic Load & thermal control. ✓

2 layer PCB - LAB only provide 1 & 2 layer PCB manufacture

↓
Impossible - since cannot make no cross tracks on the board

Try 2 layer PCB

separate Electronic Load & Thermal Control

LCD Display

- 1/4 stage
- $[V_{out+} - V_{out-}]$ outside
- $[V_{ref} - CC/CR]$
- $[I_d - \text{from } V_{sense}]$ Arduino

↓
 $V_{sense}/\text{Gain}/R_{power}$

LCD Display

- Temp - 1/4 stage
- Fan on/off

outside pin

12V power GND
5V power GND
SDA & SCL

one & 4 stages

LM324 & AD623AN

V_{ref} filter & ADS1115


V_{ref} V_{sense}
 V_{out+} V_{out-}
differential!

Temp sensor & Temp monitor
PT1000 ADS1115

Fan Control (LM324AN)

Procedures

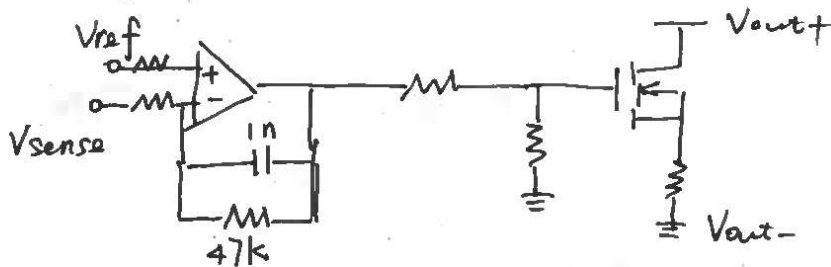① why we need error amplifier design on LM324 MOSFET comparator



Act as a filter

Avoid self-excitation, ~~two~~
More stable (whole device)

hole

if not → output - Gate Voltage



has freq since ~~input~~

there some oscillation
within the amplifier




② Why we need In-Amp AD623

more precise, accuracy

remove drift current or offset voltage in LM324

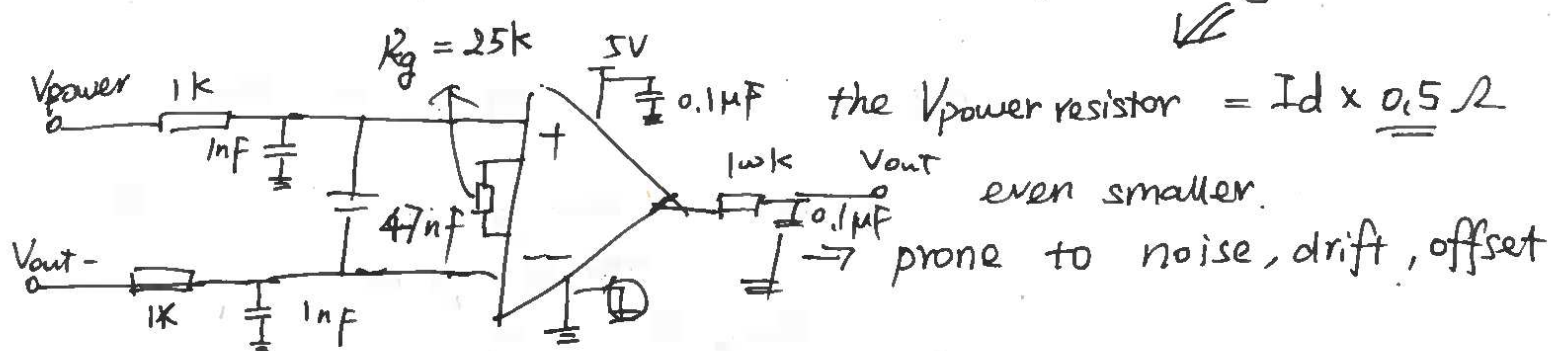achieve better control when requires very small current



AD623 Application — $G = \frac{10k}{R_g} + 1$

Calculate freq — drift — .. BW

③ Why we use ADS1115?

Arduino — analog pin — input can do voltage measurement

⇒ Show results : x x x x

Resolution : $5/1023 \approx 4.8 mV$ (too big)

Hard to V_{ref} control

Hard to V_{temp} monitor

ADS1115 . up to $\pm 6.144V$ 1 bit = $0.1875 mV$

$\pm 0.256V$ 1 bit = $0.0078125 mV$

< $0.1875 mV$ sufficient.

measure range — $6.144V \sim 6.144V$ sufficient

Best Choice

Good for test, Design usage — External device may affect original circuit (measure)

Also good at Electronic Load (give user accurate results)

the data was from 10mV to 40mV by step 1mV (2.3.4.5.6.7.8)/1023
 35mV to 505mV by step 20mV \rightarrow 39 \rightarrow (7 steps)

\swarrow
 Ins-Amp Gain = 6
 \swarrow

(7. 11. 15. 19. 24. 28. 32. 36. 40. 44. 49
 53. 57. 61. 65. 69. 74. 78. 82. 86. 90
 94. 99. 103. 2)/1023

24 \rightarrow (24 steps)

60mV to 240mV by step 6mV

each 1mV \rightarrow map to 2 steps in PWM.

Resolution was. 4.8mV \rightarrow 1.6mA at Current. \rightarrow 1023 - timerOne (10 bits)

In-Amp \Rightarrow Resolution now ~~4.8mV~~ $\frac{4.8mV}{6} = 0.8mV \rightarrow 1.6mA$ at Current.

Extension - PWM servo driver PCA 9685 12-bits - 4096 steps.

$\frac{3.3V}{4096}$
 \uparrow

give it lower value to gain high resolution. \rightarrow 0.8mV resolution

In-Amp $\Rightarrow \frac{0.8057}{6} \Rightarrow 0.1343mV \Rightarrow 0.269mA$

Another 6 times more resolution gained.