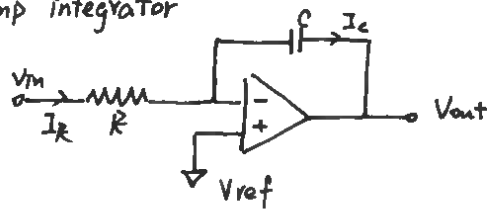


op-amp integrator




$$I_C = C \cdot \frac{dV_C}{dt} \rightarrow Q = C \cdot V_C$$


DC: Capacitor - short circuit

High freq: Capacitor - open circuit

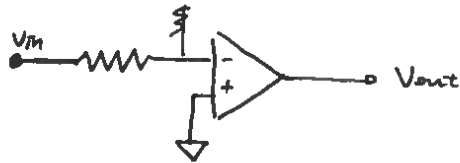⇒ set → Low freq at V_{in} : V_{out} & I_{Rshunt} remain the same (no oscillation)



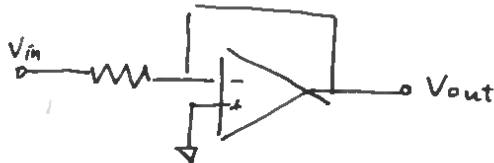⇒ High freq at V_{in} : V_{out} has ripple (the buck converter case)



Response time: RC . (short T_{RC} - response quicker)

$T_{on} < RC$
charge time

$$\frac{V_{out}(s)}{V_{in}(s)} = -\frac{1}{RCs}$$

$$\frac{V_C(s)}{V_{in}(s)} = -RCs$$


Apply Millman's theorem at negative input:

$$V_- = \frac{\frac{V_{in}}{R} + jC\omega V_{out}}{\frac{1}{R} + jC\omega} \rightarrow \text{Transfer function: } V_{in} = -jRC\omega V_{out} \Rightarrow \frac{V_{in}}{V_{out}} = -jRC\omega$$

($V_- = 0$)

Gain dB
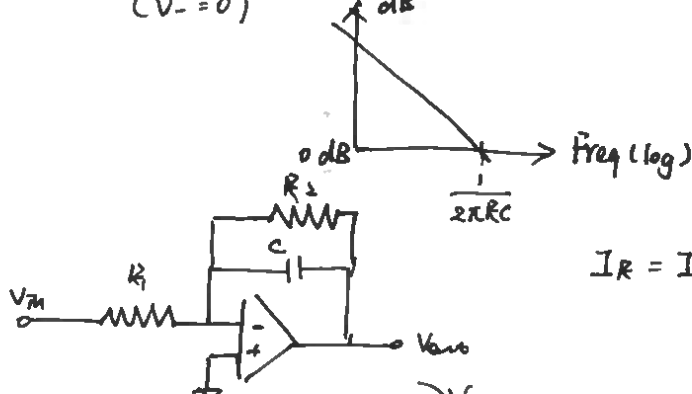
$$T = \frac{-1}{jx} \quad (x = \frac{\omega}{\omega_0}, \omega_0 = \frac{1}{RC})$$



$$I_R = I_C$$

(close loop gain, $-R_2/R_1$ when DC input.)

$$C \cdot \frac{dV_C}{dt} = -\frac{V_{in}}{R}$$

$$C \cdot \frac{dV_{out}}{dt} = -\frac{V_{in}}{R}$$

$$C \cdot s \cdot V_C(s) = -\frac{V_{in}(s)}{R}$$

$$\frac{V_C(s)}{V_{in}(s)} = -\frac{1}{CSR} = -\frac{1}{CRS}$$


(Limitation: DC components in V_{in} easy to be saturate (offset voltage))

$$C \cdot \frac{dV_C}{dt} + \frac{V_C}{R_2} = -\frac{V_{in}}{R_1}$$

$$C \cdot s \cdot V_{out}(s) + \frac{V_{out}(s)}{R_2} = -\frac{V_{in}(s)}{R_1}$$

$$(Cs + \frac{1}{R_2}) \times V_{out}(s) = -\frac{V_{in}(s)}{R_1}$$
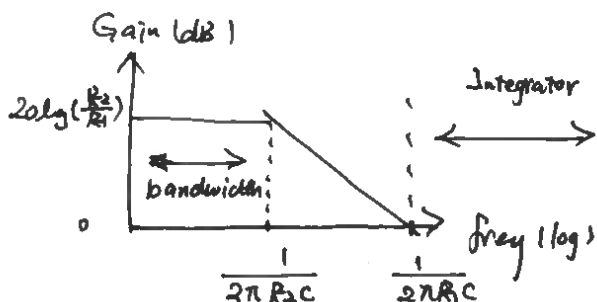
$$\frac{V_{out}(s)}{V_{in}(s)} = -\frac{1}{R_1} \times \frac{1}{Cs + \frac{1}{R_2}} = -\frac{\frac{R_2}{R_1}}{RCs + 1}$$



Now input signal $\rightarrow I_D \cdot 10m\Omega$

$$I_D \cdot 0.01\Omega$$

0.1mV reference voltage $\rightarrow 0.1A \cdot 0.01\Omega$
 $\rightarrow 9mV$

$$R_2/R_1 = 1 \text{ or smaller}$$

$\frac{1}{R_2 C} \rightarrow$ Bandwidth for R_2/R_1 gain

$$330k \sim 330k \sim 120k$$

$$330k \sim 2.25M$$

$$\frac{330k \sim 2.25M}{4} \quad 2250k$$

$$2.25 \times 10^6 Hz = \frac{1}{R_2 C}$$

$$C = 1\mu$$

$$m \mu n = p$$

$$in \times f$$

$$= \frac{1}{R_2 \times 10^6}$$

$$R_2 = \frac{1}{2.25 \times 10^6 \times 10^{-11}}$$

$$= \frac{10^3}{2.25}$$

$$= 444.4\Omega$$

$$\text{if } C = 10p = 1 \times 10^{-11} C$$

$$R_2 = \frac{1}{2.25 \times 10^6 \times 10^{-11}}$$

$$= 0.444 \times 10^5$$


$$= 44.4k\Omega$$

$$R_1 = 9.7\Omega$$

$$\text{if } R_1 = 10k\Omega$$

$$R_2 = 45560k$$

$$= 45M\Omega$$

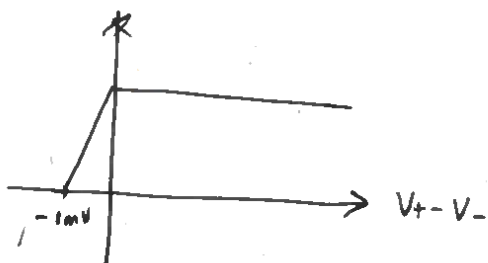

$$V_{ce} = V_c$$

$$V_{ce} = 5V \quad 5/0.1mV$$

$$= \frac{5000}{0.1} = 50000 \text{ Gain}$$

$$105mV \rightarrow$$

$$0 \sim 0.1mV \Rightarrow 4.1V \text{ output.}$$

$$\frac{4.1}{0.1mV} = 4556 \text{ gain}$$

$$\text{output } 4.1V$$

$$\text{gain } \frac{4.1V}{0.1mV}$$

$$\text{gain} = 120dB$$

$$20 \log(x) = 120$$

$$\log(x) = 6$$

$$x = 10^6$$

$$1M$$

$$10M \rightarrow$$

$$10M \leftarrow$$

$$\frac{100\Omega}{10\Omega}$$

$$5 \times 10^4$$

$$\text{if } C = 1p = 1 \times 10^{-12}$$

$$C = 0.1p$$

$$R_2 = 444k\Omega \Rightarrow 4440k$$

$$R_1 = 9.7\Omega = 10m\Omega \Rightarrow 1000\Omega$$

$$\Rightarrow 0.1V \text{ ripple} \rightarrow 10m\Omega$$

$$\frac{0.1}{10m\Omega} = \frac{0.1}{0.010\Omega} = 10A$$

$$9.1V \rightarrow 1.044 \sim 0.954A$$

$$\text{ripple } 0.09A$$

$$V = 0.09 \times 0.010\Omega$$

$$= 9 \times 10^{-4} V$$

$$= 4.5 \times 10^{-4} V$$

