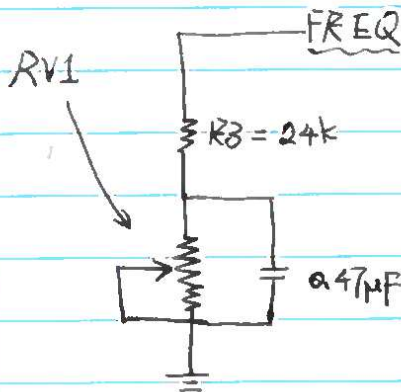


2020/06/22

Components that need replacement:

RV1 RV2 RV3 RV4  
 freq ITH setpoint  
 3362P-1-508TLF 3362R-1-222  
 50k $\Omega$  2.22k $\Omega$



If RV1 = 0 $\Omega$  (0 ~ 50k $\Omega$ )

FREQ voltage ~ 0.3V to INTV<sub>CC</sub>  
 5V 5.2V

Input Voltage 5V → ~ 5V

$$I = \frac{5}{24k} \approx 0.2083 \text{ mA} \quad \text{or INTV}_{CC} = 0V$$


Oscilloscope check INTV<sub>CC</sub> = 5V

$$I = 0.2083 \text{ mA}$$

MAX 53pS → max current to any input  
 50mA

~~ITH~~ ITH pin  $\frac{0.52}{2k}$   
~~480mV~~ 480mV { 520 mV } depends on gain  
 4mV

Operating voltage 0 ~ 5.25V

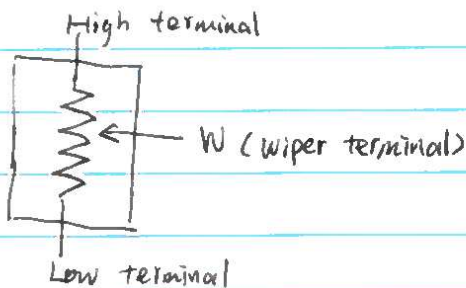

Control pin { ADDR0  
 SDA → serial data line  
 SCL → serial clock line

I<sup>2</sup>C INTERFACE

Clock = 400kHz → generated by master

SDA → byte the data word  
 for address


pull up resistor 4.7k $\Omega$

SCL ↑

Single

Start ... Stop

8 bits

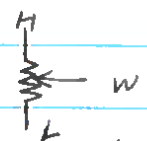Voltage divider mode  $\rightarrow$    $\Rightarrow$  Code Hex: FF ~ 000  
 Variable Resistor mode  $\rightarrow$  5, 10, 50k $\Omega$  256 Tap

$R_{wiper} = R_w = (V_w - V_h) / I_w \rightarrow 25 \sim 100 \Omega$

Charge pump disabled  $\rightarrow$  Terminal voltage rang  $0 \sim V_{DD}$

SCL freq-max = 400kHz (clock)


setup time for START = 0.6  $\mu$ s

MCP413X / 415X / 423X / 425X

$\rightarrow$  Single Potentiometer or Dual Potentiometer

Setpoint RV3, RV4

Sn74VCI63157  $\rightarrow$  B1 & B2

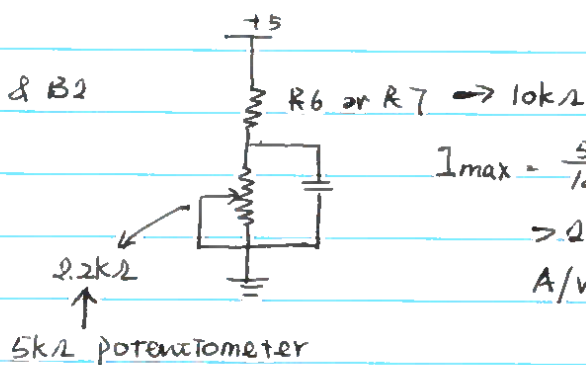

$$I_{max} = \frac{5V}{10k} = 0.5 \text{ mA}$$

$> 0.5 \text{ mA}$  maximum

A/W/B

B1 & B2 with I/O

Set High to enable

Set Low to enable

Connect

B2  $\rightarrow$  A

B1

S signal controlled by IOT 33  
 (Switch)

SyncBack  $\rightarrow$  High voltage switching


Capselect  $\rightarrow$  High V high I

LC-MODE

Sn74VCI63157

Freq

000  
000

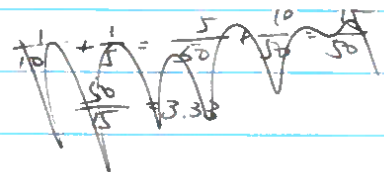

replaced by single pole triple-throw analog switch & with enable input

NX3L4357

E

S1

S0

Control Y0/Y1/Y2 = 2

$B_5 = 0 \sim 5V$   
 $5.2V$

$$\frac{1}{700ns} \rightarrow \text{freq.}$$

1.38 MHz

1.38 MHz

$$320 \sim 1300 \text{ kHz}$$

$$\frac{1}{1.45 \mu s} = 0.6897 \text{ MHz}$$

$$\frac{1}{708ns} = 1.4 \text{ MHz}$$

$$30.4ns + 3.18 \mu s$$

$$3180ns$$

$$2710ns \rightarrow$$

$$311kHz$$