

2022/06/21

~~Q1~~ Duty cycle, Inductor current ripple & Capacitor ripple measurement.


Q1. Relation between  $V_{in}$ ,  $V_{out}$ , duty cycle - In Continuous Mode.

$D \neq \frac{V_{in}}{V_{out}}$   
 $\uparrow$   
 discover from signal

$D > \frac{V_{in}}{V_{out}}$  but linearly related.  
 loss contained.

Discontinuous.  $\frac{V_{in}}{V_{out}} = \frac{D}{D+D}$

$\Delta$  time for  $I_L = 0$

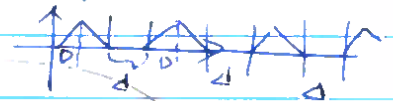

Q2

$$\Delta I = \frac{(V_{in} - V_{out}) \cdot t_{on}}{L}$$

Inductor current vs duty cycle.  
 ripple


$$= \frac{V_{out} \times t_{off}}{L}$$

$$= \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{2} \times (1-D) T$$

$$= \frac{D(1-D) \cdot T \times V_{in}}{L}$$

$$= (D - D^2) \cdot T \times \frac{V_{in}}{L}$$

quadratic

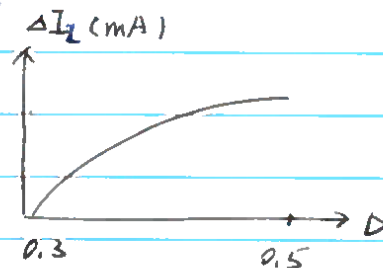

Q2

Inductor current ripple  $\Delta I$  vs load current

$$\Delta I = \frac{I_o R}{L} \times t_{off} = \frac{I_o R}{L} \times (1-D) T = \frac{I_o R}{L f} (1-D)$$

$\downarrow$

change little

unchange

most effective

$\Delta I$  will change since  $I_o$  change

But basically remain the same

Inductor current ripple  $\Delta I_L$  vs switching frequency

$$\Delta I_L = \frac{I_o R}{L f} (1-D)$$

$\uparrow$

Inversely proportional

Q3.

$\Delta V_C$  vs  $V_{in}$

$\Delta V_C$  vs  $I_{out}$

$\Delta V_C$  vs  $f_s$

Capacitor current ripple  $\rightarrow (V_{out} - V_{avg} R_{sense})$  for AC mode

coupling AC mode

$$\Delta V_C = \frac{Q}{C} = \frac{V_o(1-D)}{8LC} \times T^2 = \frac{D(1-D) \cdot V_{in}}{8LC} \times T^2$$

$V_{in}$   $\uparrow$   $f_{req} \frac{1}{f_s^2}$

$$= \frac{I_o R(1-D)}{8LC} \times T^2$$

$I_{out}$

$\Delta V_C$  proportional to  $I_{out}$ , to  $V_{in}$

$\Delta V_C$  Capacitor ripple  $\propto V_{in}$

unchange to  $I_{out}$  since  $V_o = I_o \times R$   
 $\uparrow$   
 change

$$\Delta V_C = \frac{(1-D) \cdot D \cdot V_{in}}{8LC \cdot f_s^2} = \frac{V_{out}(1-D)}{8LC \cdot f_s^2} = \frac{I_o \times R_L (1-D)}{8LC \cdot f_s^2}$$

Q4.  $\Delta V_C = \frac{V_{out}(1-D)T^2}{8LC}$

$$\frac{\Delta V_{C1}}{\Delta V_{C2}} = \frac{C_2}{C_1}$$

$\uparrow$   
CapSelect.

~~Q4.  $\Delta V_C = \frac{V_{out}(1-D)T^2}{8LC}$~~

Discontinuous Operation  $\rightarrow$  Sync Buck - off

Q1 33.2 resistor  $\rightarrow$  Boundary Condition.  $\rightarrow$


Increase  $R_L$  see  $V_{out}$ ,  $I_L$ , Duty cycle,  $I_o$

verify

Inductor current

Switch

$I_L$

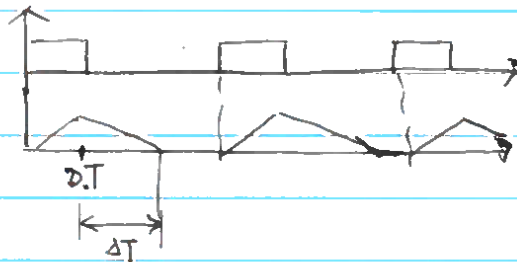

Q2

$$\Delta = \frac{2I_{out}L}{DT(V_{in} - V_{out})} - D$$

$$\Rightarrow I_{out} = \frac{DT(\Delta+D)(V_{in} - V_{out})}{2L} = \frac{DT(V_{in} - V_{out})}{L} \times \frac{(\Delta+D)}{2}$$

$$= \frac{DT(V_{in} - D V_{in})}{2L} \times (\Delta+D)$$

$$\frac{V_{out}}{V_{in}} = D$$

$$V_{out} = D \cdot V_{in}$$

$$= \frac{(DT V_{in} - DT \cdot V_{in}) (\Delta+D)}{2L}$$

$$= \frac{(DT V_{in} - D^2 T V_{in}) (\Delta+D)}{2L}$$

$$= \frac{T V_{in} (D - D^2) (\Delta+D)}{2L}$$

$$= \frac{DT V_{in} (1-D) (\Delta+D)}{2L}$$

$$(1-D)(\Delta+D)$$

$$= \Delta - \Delta D + D - D^2$$

$$=$$

$$I_{out} = \frac{V_{in} T}{2L} \times D \times \Delta$$

$$\frac{V_o}{V_d} = \frac{D}{\Delta+D} = \frac{V_o}{V_{in}} = \frac{D}{\Delta+D}$$

$$I_{out} = \frac{DT(\Delta+D)(V_{in} - V_{out})}{2L} \quad (1 - \frac{D}{\Delta+D})$$

$$= \frac{DT(\Delta+D) V_{in} (1 - \frac{D}{\Delta+D})}{2L}$$

$$= \frac{DT(\Delta+D) \times (\frac{\Delta}{\Delta+D}) \times V_{in}}{2L} = \frac{V_{in} \cdot T \cdot \Delta \cdot D}{2L}$$

$$= \frac{V_{in} T \Delta D (\Delta+D)}{2L} = \frac{V_{in} T \Delta D}{2L}$$

Q3

verify

below 20V input  $\rightarrow$  LED red lighted up & No output.

## Advanced Performance & Features

### Q1. Load Regulation.

$V_{out}$  at light loads, medium loads, heavy loads

### Q2. Current limiting

#### 2.1. LTC1800 Current limiting function.

Sense+ Sense -  $I_{LIM}$ .

↓  
Hatched.  $I_{max} = 75mV$  threshold.

$$R_{sense} = 0.015 \Omega \rightarrow \frac{75mV}{0.015} = \frac{0.075}{0.015} = 5A \text{ max current limiting}$$

#### 2.2. $R_{load}$ made smaller and smaller

$V_{out}$  drop ~~exp~~ dramatically ✓

#### 2.3. Suddenly short circuited.

→  $V_{out}$  → reduce above zero oscillate → zero

→  $I_{out}$  → Max Limit  $5A$

$$R_L = \frac{V_{out}}{I_{load}} = \frac{3.3V}{50mA} = 66 \Omega$$

### Q3 Light Load operation → LTSpice since PCB not function.

#### 3.1 Light load operation mode → impact. operation & Eff & performance

① Burst Mode. — SGND 68.1% eff.

↓  
 $V_{out}$


LTSpice

study  
modes  
operation

PLLIN/Mode ———— 100k


Inductor current. 

Switch. 

$V_{out}$  

② Pulse-skipping. 135%

PLLIN/Mode ———— 5V  
100k

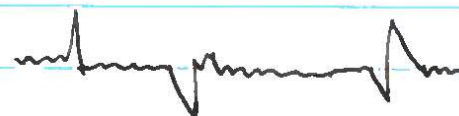$I_L$  

③ Force - Continuous. 12.4%

→ INTVcc

Burst Mode — highest efficiency.

Forced Continuous Mode — Output ripple independent of load current.

Pulse Skipping Mode —  $I_L$  not allowed to reverse.

Higher efficiency than forced continuous (low current).

Low output ripple

Low audio noise.

Cannot do these mode on PCB since  $R_{sense}$  doesn't connect to sense + sense -

Q4 Impact of Feedback Controller gain on Steady-State & Transient.

ITH pin  $\rightarrow$

( $V_{FB}$  & Track/SS)

controls  
 $V_{out}$

4.1 How the feedback gain is adjusted by PCB.

study control system  
Feedback loop.

$RV2 \leftrightarrow R_c$  (on LTC78W internal circuit)

4.2. Feedback gain impacts the steady-state output voltage regulation.

$\uparrow$  cause ripple in  $V_{out}$   $\uparrow$

But  $V_{out,rms}$  same

Check by oscilloscope  $\checkmark$

How to set up  
Oscilloscope

4.3 Feedback gain impacts the transient output voltage regulation

step in output voltage

Setpoint from 2V to 4V (switches)

Problem = How to operate in "single mode" in Oscilloscope?

(2022/06/22) Figure it out tomorrow.

~~Step~~  $\star$  step in output voltage reference  $RV3$  &  $R_{14}$  switches

step in  $R_2 \rightarrow$  load resistance  $\uparrow$

More than 2 adjustable resistance same design?

Feedback gain increase  $\rightarrow$  Transient time ~~more~~ decrease

But overshoot increase

was  Now 



#### 4.4. Output capacitance size impact Transient response

CapSelect  $\uparrow$  ~~longer~~  $\downarrow$  shorter transient time  $\downarrow$  less overshoot  $\downarrow$

#### 4.5. Using Fan bank as a load / compared to resistive load.

DC motor  $\rightarrow$  Gap at beginning

$\downarrow$   
DC  $\rightarrow$  0 resistance

$\rightarrow$  ~~shorter~~ ~~transition~~ transition time  $\checkmark$   
Shorter (response quickly)

Three modes {  $I_{out}$   $V_{out}$   $E_{ff}$   
 $\downarrow$   
Burst

Burst  $I_{out} \downarrow$   ~~$V_{out}$~~   $E_{ff} \uparrow$

Forced Continuous - less ripple  $\Delta V_{out}$

Question: Single Mode in Oscilloscope - Transient

$\checkmark$  step in  $V_{out}$  - reference - achieved by switches

$\checkmark$  step in  $R_L$  - connection of 2 R

solved

(RUN)

Source  $\rightarrow$  trigger  $\rightarrow$  channel 3  $\rightarrow$  Trigger 3V  $\rightarrow$  Switch  $\rightarrow$  Capture  
 $\uparrow$   $\uparrow$   
 $V_{out}$  from 2-4V