

2022/06/11P

LTSpice ~~plotted~~ plot, step'd, meas data from Spice error log.

data vs step
selected ~~trace~~ trace x-axis

can be ~~ex~~ changed to other data

For example: Eff vs I_{out}

How to vary the output current when V_{in} = 10V V_{out} = 3.3V.

R_L = 10.2 ?

I_{out} = mean value of I_L →

$$G_p(s) = \frac{V_o}{i_L} = \frac{R(1 + s\tau_{esr})}{(1 + sRC)} \Rightarrow \text{plant}$$

Transfer function ★ need to learn) R_L

pole location

single pole

→ explore later

Q_{out}
Freq

Q1 ⇒ ① Input V = 10V V_{out} = 3.3V.

R_L → 0 ~ 33Ω


I_{out} = 0.5 ~ 4A

Part or $\frac{P_{out}}{P_{in}} = \text{Eff}$ VS I_{out}.

$$\text{Eff} = 1 - \frac{P_{loss}}{P_{in}}$$


P_{loss} = I² · R_{ds} conduction.

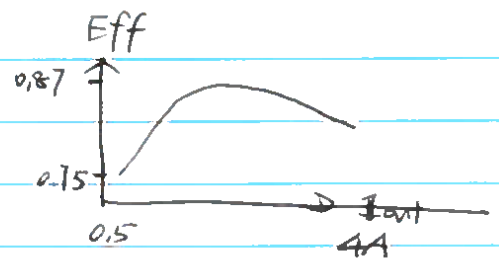P_{loss} = P_{conduction loss} + P_{switch loss}



Q2 ⇒ Almost the same: Eff: ~~56.5%~~ 56.5% ~ 84%


0.5 ~ 3.66A

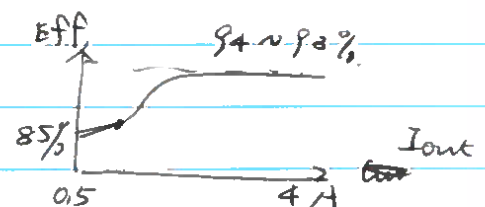

Q3. Switching impacts converter efficiency.

F: 31.8.1kHz ~ 11.8kHz

Eff = 0.868 ~ 0.842

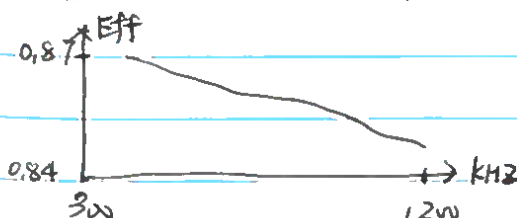

Switching Losses = (E_{on} + E_{off}) f_s


f_{req} ↑ switching losses ↑

P_{switchloss} ∝ f_s

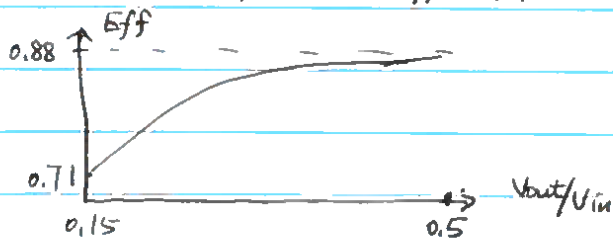Q4. $\frac{V_{in}}{V_{out}}$ ratio impact Efficiency.

$\frac{V_{out}}{V_{in}} = \frac{3.3}{10} = 0.33 \rightarrow$ duty cycle \rightarrow higher ratio \rightarrow higher efficiency

$0.15 \sim 0.46 \Rightarrow \eta = 71\% \sim 88\%$



during T_{off} , Inductor convert Energy to electrical energy (output)
This process is lossless
less T_{off} better efficiency
high D better eff.

Q5. LTSpice Gate resistor impacts converter's Efficiency

R_g : 0.1, 1.6, 3, 5, 1 \rightarrow 37.07%

P_{out}/P_{in} : 87.28%, 80.66%, 62.097%

As gate resistance increase, the switching process slow down, yielding increasing switching loss. At same time, drive loss increase.

Q6. $R_g \uparrow$ Voltage & Current overshoot of MOSFET \downarrow
the conduction time longer.

Gate resistor impact on Switching performance of MOSFET

Overshoot \downarrow smaller Oscillation \downarrow decrease
 \rightarrow Transition time longer \uparrow efficiency \downarrow (switch losses) (resistance loss).

Q7. SyncBuck from "ON" to "OFF"

Bottom MOSFET \rightarrow Diode

Synchronous Non-Synchronous

Efficiency decrease since $P_{switchloss}$ higher in Diode

$\frac{17.338}{17.22} = 83.26\% \uparrow$ $\frac{14.28}{18.42} = 77.52\% \downarrow$

2022/06/20

Arduino Nano 33 IoT

→ 3.3V device - Jumper - USB - VUSB - sending 3.3V.

(SAM D21G 32-bit microcontroller) 48MHz, Internal Real-time clock

(Wifi & Bluetooth using u-blox NINA-w101 module) 2.4 GHz Antenna.

LSM6DS3 I2C Inertial measurement unit)

{ ADC5 - SCL internal pull-up
ADC4 - SDA internal pull-up

Modulation capable pin: PWM: D2 D3 D5 D6 DP D10 D11 D12

Library: WiFiNINA - Wifi

Arduino LSM6DS3 - Inertial measurement

Arduino RTCZero - Real time Clock

Arduino BLE - Bluetooth

Download Arduino IDE

Json Format → Example code

Arduino code → Example

pin configuration.

Arduino Nano 33 IoT

★ → deserialization message (Json format)

→ set pin output (High/Low)

★ Read Practicle/pendduino / Example code.