

Problem 1: Op-Amp stable operation should maintain gain > 1 (simulation error)

Solution: upgrade sense resistor value.

Afterwards, we can use differential amplifier to amplify voltage across small value sense resistor

One of these allegro sensors is recommended for my circuit:

<https://www.allegromicro.com/en/products/sense/current-sensor-ics/zero-to-fifty-amp-integrated-conductor-sensor-ics>

Main task:

Study performance of Op-Amp LM741 and FDS9926A dual N-channel MOSFET for building test circuit.


The frequency chosen is 1KHz, which is suitable for LM741 (with around 200KHz bandwidth product)

FDS9926A: spice model found from


[https://www.onsemi.com/design/resources/technical-documentation?](https://www.onsemi.com/design/resources/technical-documentation?rpn=FDS9926A#ZHQ9TW9kZWxzO3N3PUZEUzk5MjZBO3N0PXR5cGU7c2Q9ZGVzYzs=)

[rpn=FDS9926A#ZHQ9TW9kZWxzO3N3PUZEUzk5MjZBO3N0PXR5cGU7c2Q9ZGVzYzs=](https://www.onsemi.com/design/resources/technical-documentation?rpn=FDS9926A#ZHQ9TW9kZWxzO3N3PUZEUzk5MjZBO3N0PXR5cGU7c2Q9ZGVzYzs=)

The same structure

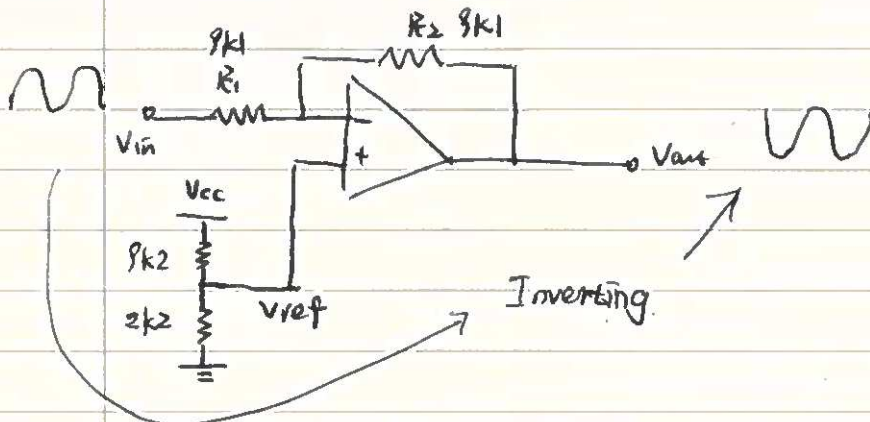
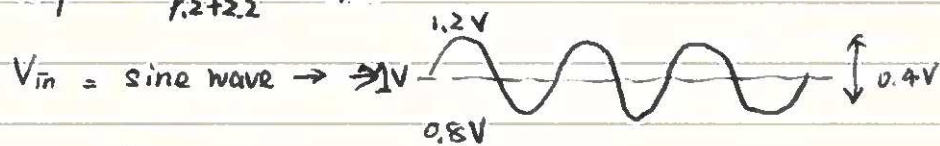
$$V_{ref} = 5 \times \frac{2.2}{9.2 + 2.2} \approx 0.965$$




$$f_{req} = 322.2 \text{ kHz}$$

$$V_{out} = 1.8 \text{ N } 2 \text{ V sine } f_{req} = 322.6 \text{ kHz}$$

$\updownarrow 0.2 \text{ V}$
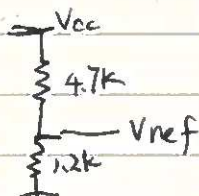
$$V_{out \text{ offset}} = 1.9 \text{ V} \rightarrow 2.2 \times 0.965 = 1.930 \text{ V}$$




$$V_{ref} = 1 \text{ V}$$


$$V_{in} = 1 \text{ V offset } 0.4 \text{ mV amplitude}$$

$$V_{out} = 1.9 \text{ V offset } 0.2 \text{ mV amplitude}$$

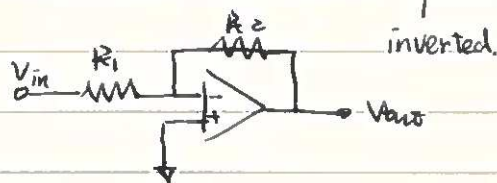
★ Gain calculated wrong: for inverting amplifier $A_v = -\frac{R_2}{R_1}$



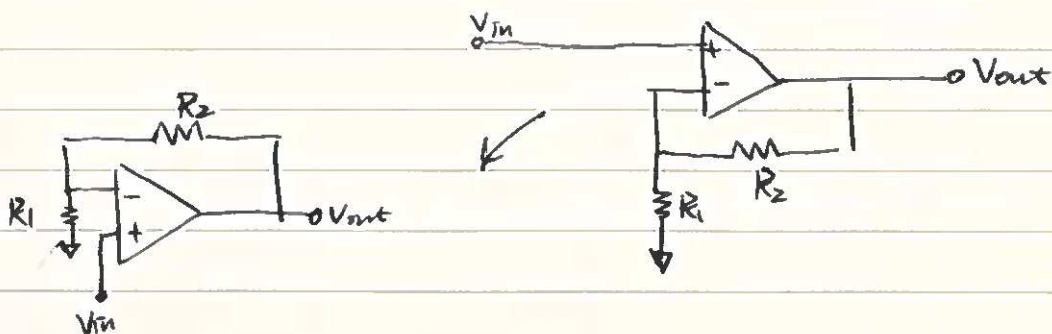for non-inverting amplifier: $A_v = 1 + \frac{R_2}{R_1}$




Verification by simplest circuit

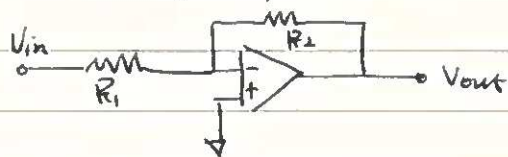

$$R_2 = R_1 = 9k\Omega$$

$V_{in} = 1V$ offset with $\pm 0.1V$ amplitude $0.9 \sim 1.1V$

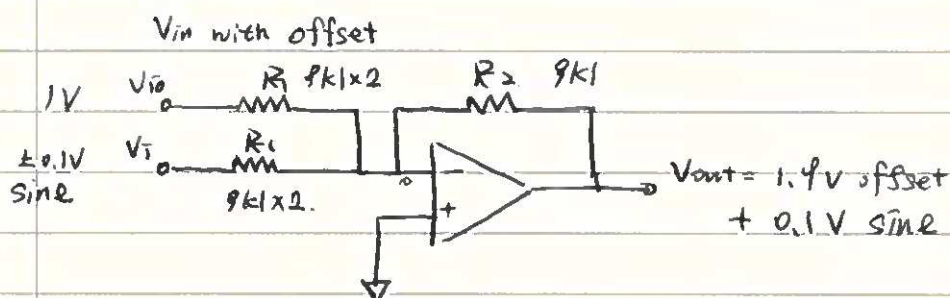$V_{out} = 1.8V \sim 2V \rightarrow$ 1.9 offset with $\pm 0.1V$ amplitude



$$\frac{V_{out} - V_-}{R_2} = \frac{0 - V_{io}}{R_1}$$

$$V_{out} = -\frac{V_{io}}{R_1} \times R_2$$

$$\frac{V_{out}}{V_{io}} = -\frac{R_2}{R_1} = -\frac{9k\Omega \times 2}{9k\Omega} = -2$$

inverting but for offset \rightarrow No effect for inverting,

$V_{out-offset} = 1.9V$ $V_{io-} = 1V$? 1.9 gain rather than 2


why

~~$9k\Omega \times 2 = 18k\Omega$~~

\Rightarrow If op-amp input is DC

lets put $V_{in} = 1V_{DC} \Rightarrow V_{out} = 1.9V$

\Rightarrow Amplification for DC input.

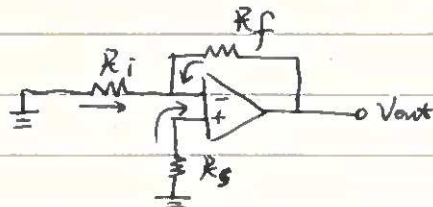

bias current $\rightarrow R_i$ & R_s doesn't match

current different at V_- & V_+

① R_i & R_s matched

\rightarrow current V_- & V_+ identical


$R_s = R_i$ parallel with $R_f \rightarrow$ DC offset

Input offset offset current

$$V_{out_offset} = A_n \times V_{os} + I_{os} \times R_f$$

noise gain

$$A_n = 1 + \frac{R_f}{R_i}$$

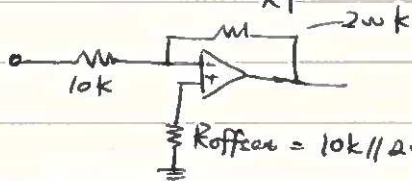

Datasheet = $V_{os} = 5mV \rightarrow LM741: 15mV$

$I_{os} = 0.1 \mu A \rightarrow 80 \sim 500 nA$

$$\rightarrow A_v = -\frac{R_f}{R_i} = -20$$


$$A_n = 1 + \frac{R_f}{R_i} = 21$$

$$\begin{aligned} V_{out_offset} &= 21 \times 5mV + 0.1 \mu A \times 20k \\ &= 105mV + 20mV \\ &= \pm 125mV \end{aligned}$$

In my case: $V_{out_offset} = 2 \times 15mV + (80 \sim 500 nA) \times 9k1$

$$= 30mV + 4.5mV$$

$$= \pm 34.5mV$$

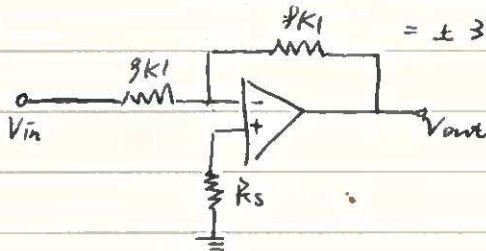


$$I_{offset} = \frac{1V}{9k1} = \frac{1}{9k} A \approx$$

$I_{output\ offset} = I_{input}$

$$\Rightarrow V_{offset} = \frac{1}{9k1} \times R_f$$

$$= 1V$$

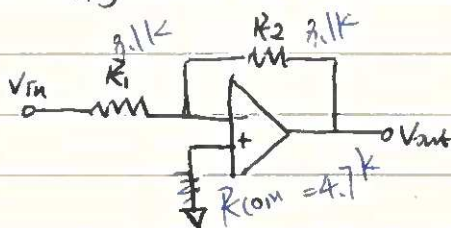Power supply should be double sided $\rightarrow \pm 15V$



$$A_v = -\frac{R_2}{R_1} = -1 \text{ gain}$$

$V_{in} = \pm 0.5V$ sine wave with 333.3 kHz

$V_{out} = \pm 0.3V$ sine wave

1.5MHz Bandwidth - typical.